Contents

1 Exercitiu $A(db) = 20 \cdot log_{10} \frac{V_i es}{V_i n}$

1

1 Exercitiu

$$\begin{aligned} R_1 &= 100~\Omega \\ C &= 3.18 \\ B &= ? \end{aligned}$$

$$F = \{1_{\overline{2}} \cdot 3.14 \cdot 100 \cdot 3.18 \cdot 10^{-6}\} = {^{\sim}500}Hz$$